

Specification:  $V_{REF} = 4V$ ,  $V_H = 10V$ ,  $V_L = -5V$

$$R_1 = 3k\Omega, R_2 = 6k\Omega$$

Question: What type of Schmitt Trigger is this?

Determine  $R_x$ ,  $V_{TH}$ ,  $V_{TL}$ ,

Hysteresis width, Draw VTC ( $V_o$  vs  $V_{in}$ )

Solution: This is inverting Schmitt Trigger

$$R_x^{-1} = R_1^{-1} + R_2^{-1}$$

$$\Rightarrow R_x^{-1} = (3k\Omega)^{-1} + (6k\Omega)^{-1}$$

$$\Rightarrow R_x = 2k\Omega$$

$$V_{TH} = V_{REF} \frac{R_2}{R_1+R_2} + V_L \frac{R_1}{R_1+R_2}$$

$$= 4 \frac{6}{3+6} + 10 \frac{3}{3+6}$$

$$= 6 \text{ V}$$

$$V_{TL} = V_{REF} \frac{R_2}{R_1+R_2} + V_L \frac{R_1}{R_1+R_2}$$


$$= 4 \frac{6}{3+6} + (-5) \frac{3}{3+6}$$

$$= 1 \text{ V}$$


$$\text{Hysteresis width} = V_{TH} - V_{TL}$$

$$= 6 - 1$$

$$= 5 \text{ V}$$

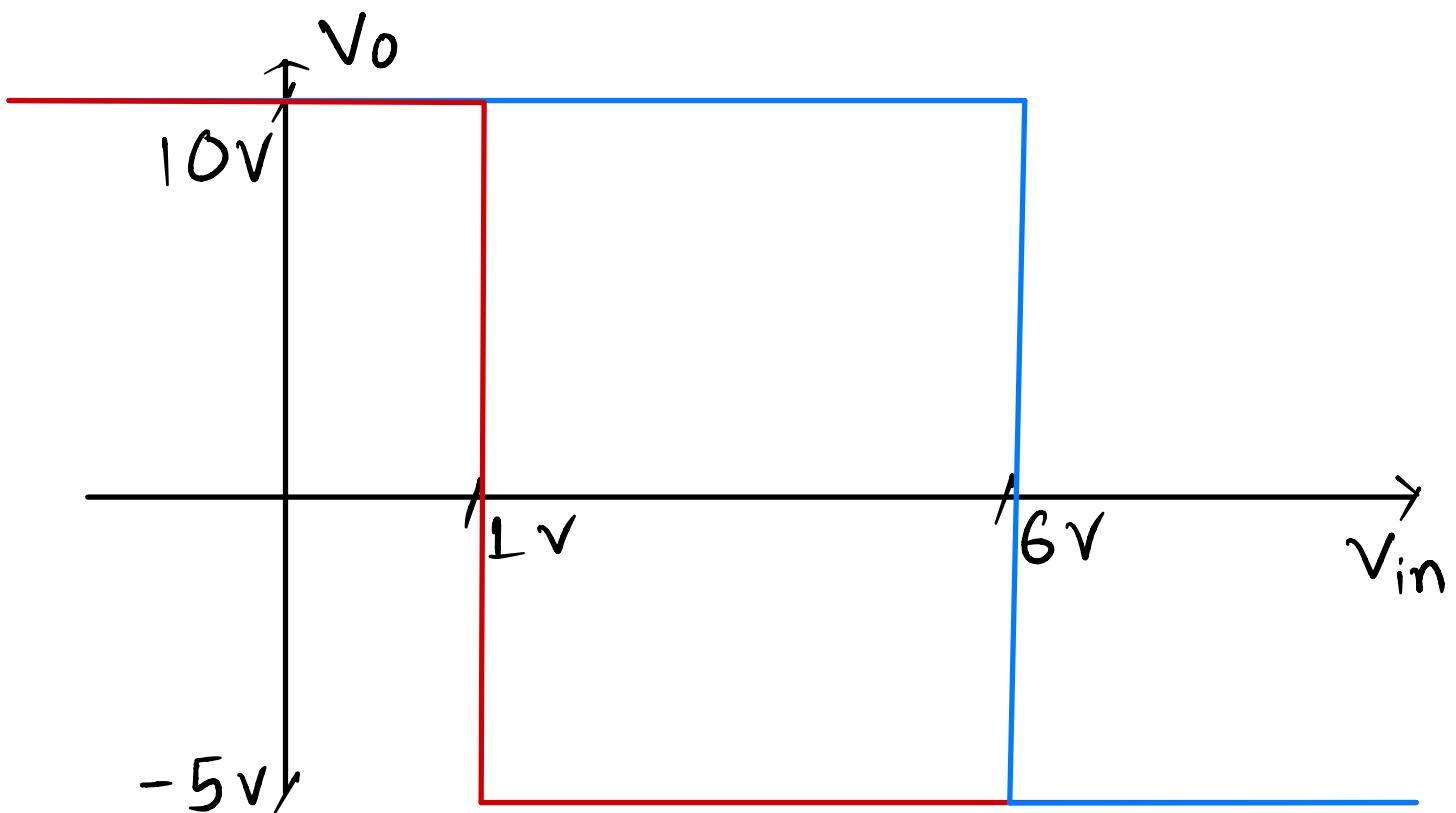

2.  $V_{REF}$

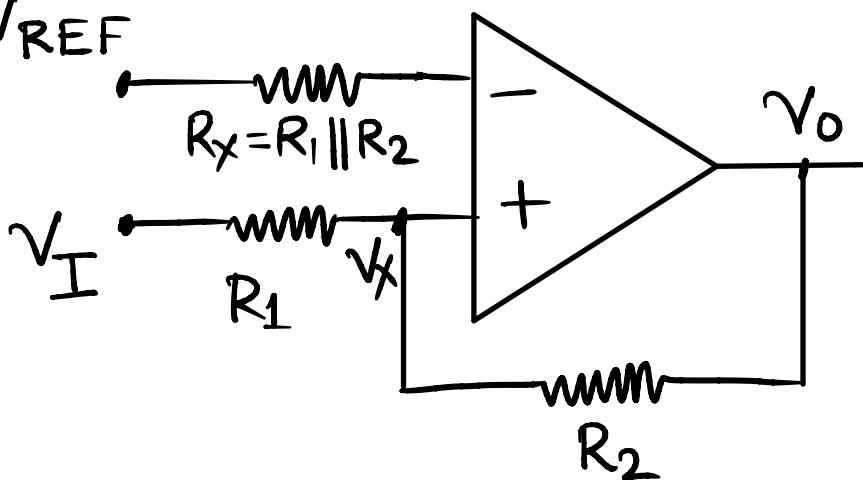

Given, Hysteresis width = 14 V,  $R_x = 3.5 \text{ k}\Omega$

Case 1:  $V_{REF} = 2 \text{ V}$  and  $V_I$  is very low (large negative voltage),  $V_x = 2 \text{ V}$

Case 2:  $V_{REF} = 4 \text{ V}$  and  $V_I$  is very high (large positive voltage),  $V_x = 25 \text{ V}$

Question: What type of Schmitt Trigger is this?

Find  $R_1$  and  $R_2$ ,  $V_H$  and  $V_L$

Solution: This is a non-inverting Schmitt Trigger

Hysteresis width

$$\Rightarrow V_{TH} - V_{TL} = \left(-\frac{R_1}{R_2}\right)V_L - \left(-\frac{R_1}{R_2}\right)V_H$$

$$\Rightarrow 14 = \left(V_L - V_H\right)\left(-\frac{R_1}{R_2}\right)$$

We know,

$$V_{TH} = V_{REF} \left( \frac{R_1 + R_2}{R_2} \right) + \left( -\frac{R_1}{R_2} \right) V_L$$

$$V_{TL} = V_{REF} \left( \frac{R_1 + R_2}{R_2} \right) + \left( -\frac{R_1}{R_2} \right) V_H$$

---

Case 1:  $25 = 4 \frac{R_1 + R_2}{R_2} + \left( -\frac{R_1}{R_2} \right) V_L \dots \textcircled{i}$

Case 2:  $2 = 2 \frac{R_1 + R_2}{R_2} + \left( -\frac{R_1}{R_2} \right) V_H \dots \textcircled{ii}$

---

$$\textcircled{i} - \textcircled{ii} \Rightarrow 23 = 2 \frac{R_1 + R_2}{R_2} + (V_L - V_H) \left( -\frac{R_1}{R_2} \right)$$

$$\Rightarrow \frac{23 - 14}{2} = \frac{R_1 + R_2}{R_2}$$

$$\Rightarrow 4.5 = \frac{R_1 + R_2}{R_2}$$

$$\Rightarrow 3.5 = \frac{R_1}{R_2}$$

$$\Rightarrow R_1 = 3.5 R_2 \\ = 7 k\Omega$$

$$\frac{1}{R_X} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$3.5 k = \frac{1}{3.5 R_2} + \frac{1}{R_2}$$

$$\Rightarrow R_2 = \frac{3.5 k}{3.5} + 1$$

$$\Rightarrow R_2 = 2 k\Omega$$

$$\textcircled{i} \quad 25 = 4 \frac{R_1 + R_2}{R_2} + \left( -\frac{R_1}{R_2} \right) V_L$$

$$\Rightarrow 25 = 4 \frac{7+2}{2} + \left( -\frac{7}{2} \right) V_L$$

$$\Rightarrow V_L = (25 - 18) \left( -\frac{2}{7} \right)$$

$$= -2 V$$

$$\textcircled{ii} \quad 2 = 2 \frac{R_1 + R_2}{R_2} + \left( -\frac{R_1}{R_2} \right) V_H$$

$$\Rightarrow 2 = 2 \frac{7+2}{2} + \left( -\frac{7}{2} \right) V_H$$

$$\Rightarrow V_H = (2-9) \left( -\frac{2}{7} \right)$$

$$= +2 V$$

3. Implement the boolean function

$$Y = \overline{AB} + C \text{ with CMOS Logic}$$

Solution :  $Z = \overline{Y} = \overline{\overline{AB} + C}$

Pull down

$$\overline{Z} = \overline{\overline{\overline{AB} + C}}$$

$$\overline{Z} = \overline{AB} + C$$

$$= \overline{A} + \overline{B} + C$$


Pull up

$$Z = \overline{\overline{AB} + C}$$

$$= \overline{\overline{AB}} \cdot \overline{C}$$


$$= AB \cdot \overline{C}$$

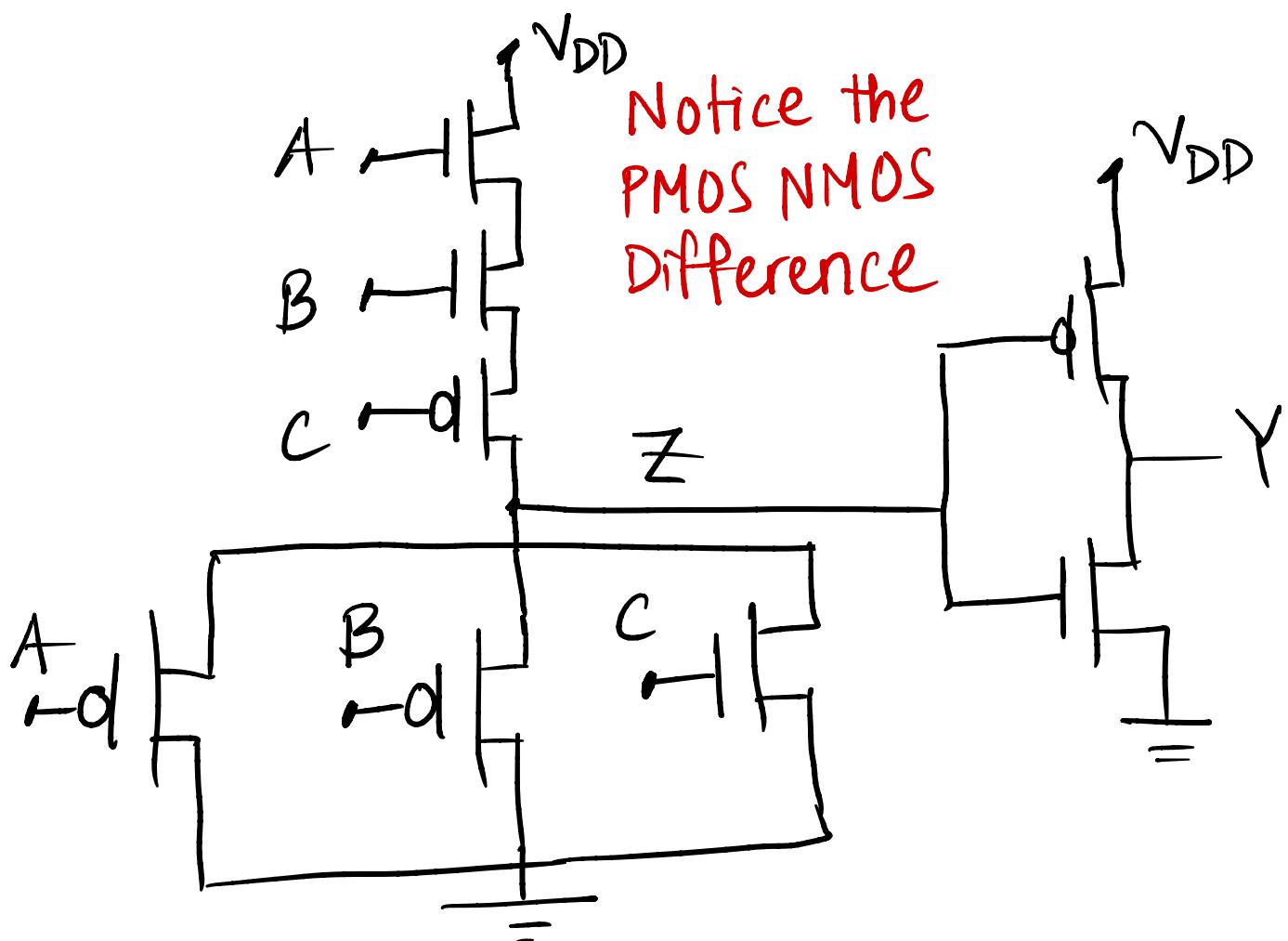Individual input with bars are PMOS and without bars are NMOS



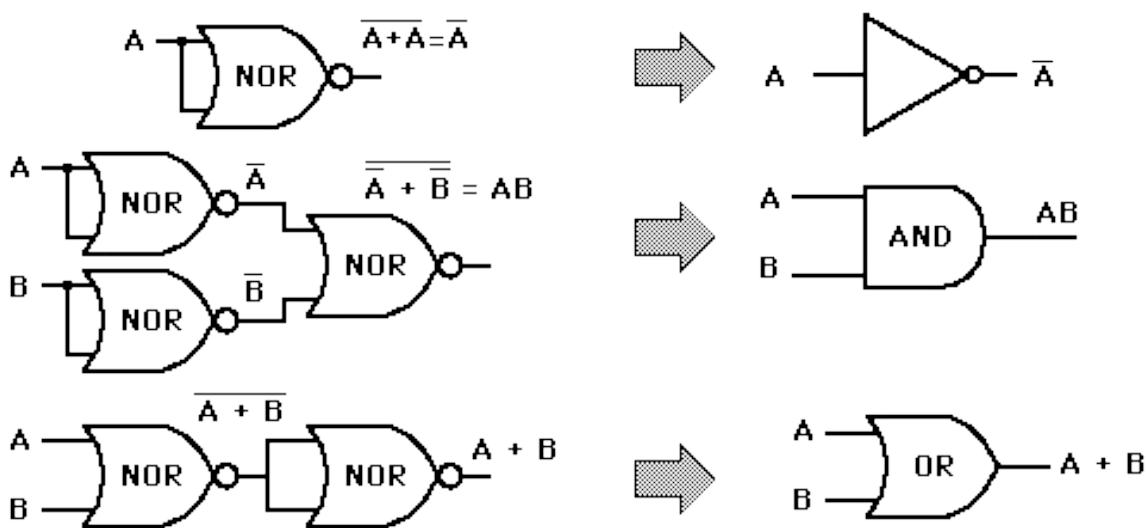
4. Implement  $Y = \overline{(A+B)} + CD$  using NOR Mosfet logic circuit

We know, NOR gate is a universal gate. We can implement AND, OR, NOT using just NOR gate



$$Y = \overline{(A+B)} + CD$$

Logic gate form:

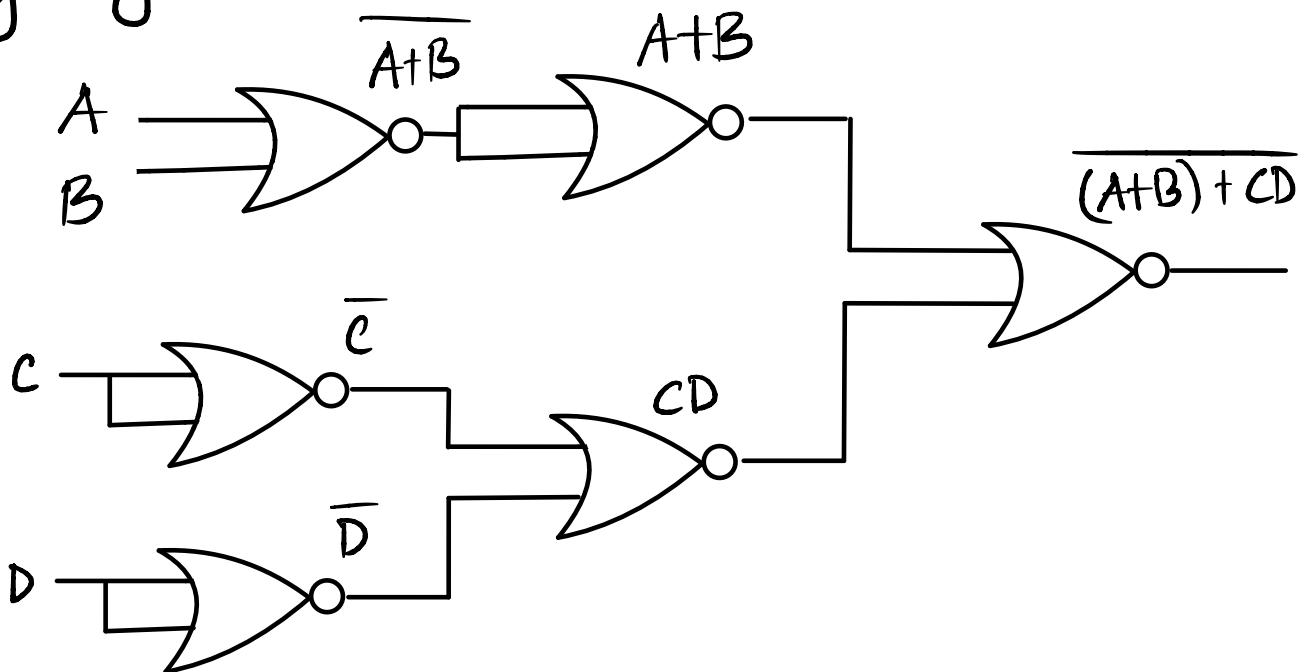

## Circuit form :

