


## Homework 8.1

Homework due Sep 2, 2022 23:59 +06 Completed

[Bookmark this page](#)

### HW 8.1.1

6.0/6.0 points (graded)

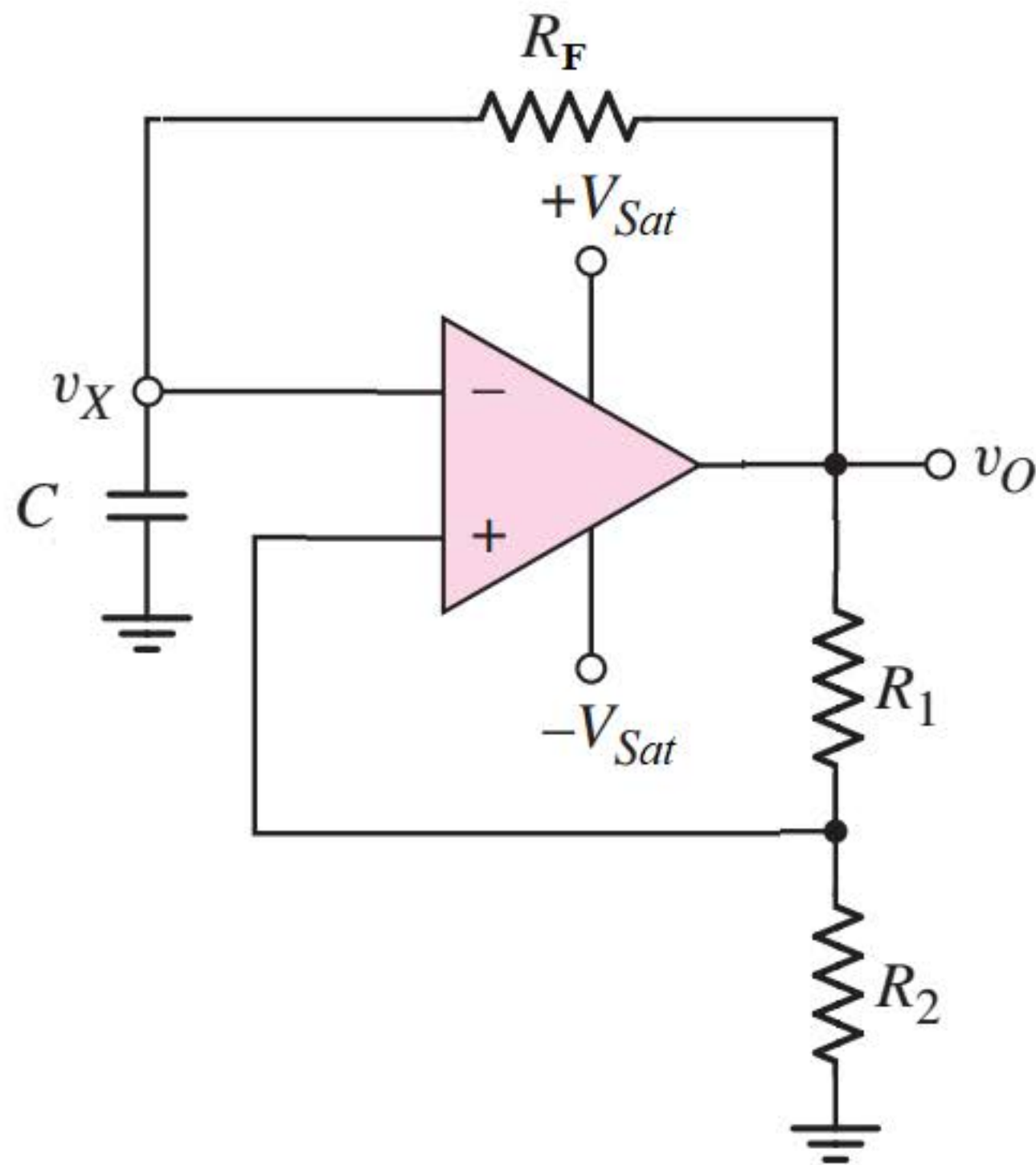

Now in the square wave generator  $R_1 = 200k\Omega$ ,  $R_2 = 172k\Omega$  and  $+V_{sat} = 20V$  and  $-V_{sat} = -20V$

Find out the upper threshold voltage.



9.2473

Find out the lower threshold voltage.



-9.2473

Find the total time period  $T$  in  $ms$  if  $R_f C = 10ms$



20.0126


# Homework 8.2

Homework due Sep 2, 2022 23:59 +06 Completed

Bookmark this page

## HW 8.2.1

5.0/5.0 points (graded)

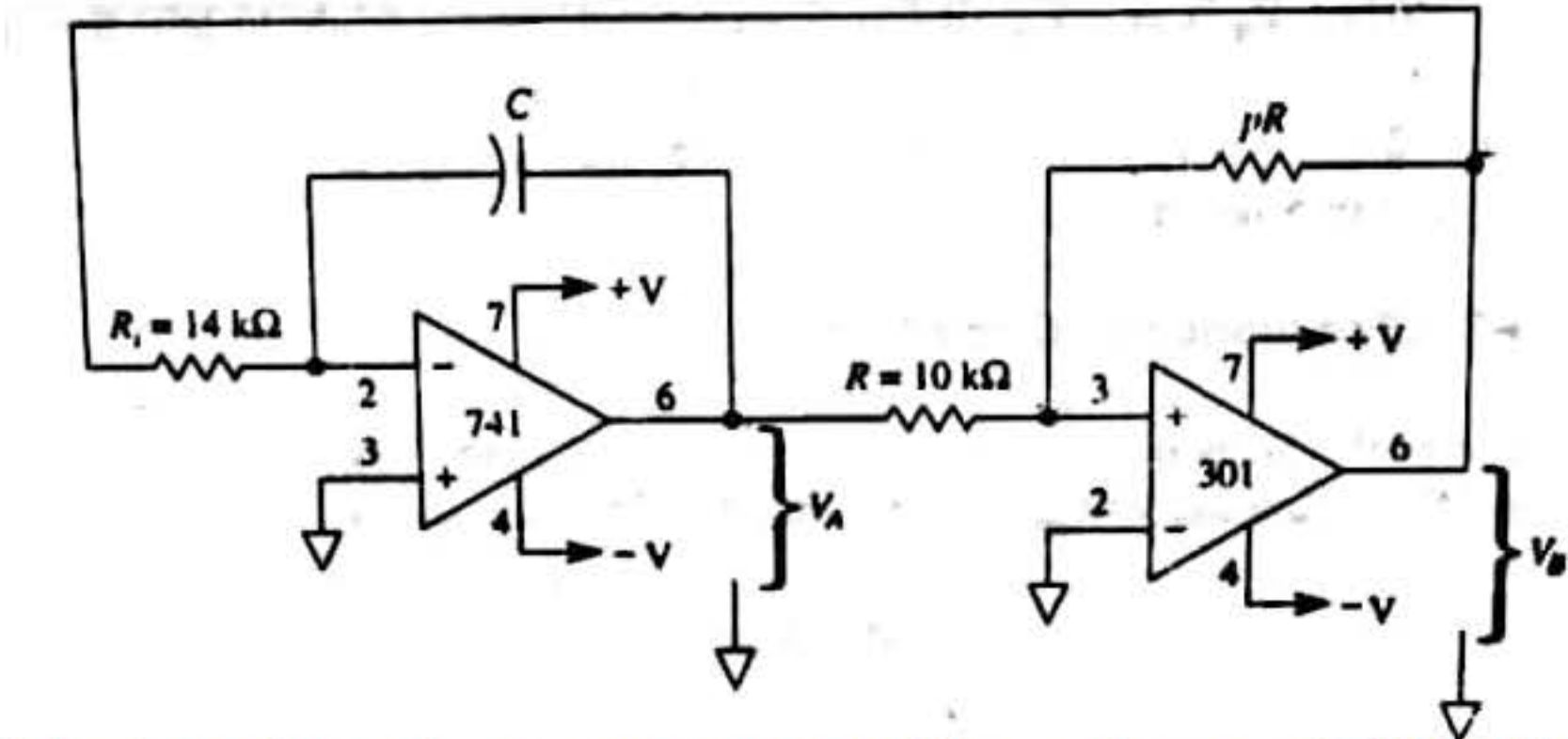

In the picture above a triangular wave generator oscillates at a frequency of  $500\text{Hz}$  with the peak value of approximately  $5\text{V}$ . Moreover, the effective value for  $+V_{sat} = 14.2\text{V}$  and  $-V_{sat} = -13.8\text{V}$ .

Calculate the required value for  $pR$  in  $k\Omega$

✓

27.6

Calculate the required value for  $C$  in  $\mu\text{F}$

✓

0.1


Save Show answer

Submit

You have used 1 of 5 attempts

## HW 8.2.2

5.0/5.0 points (graded)

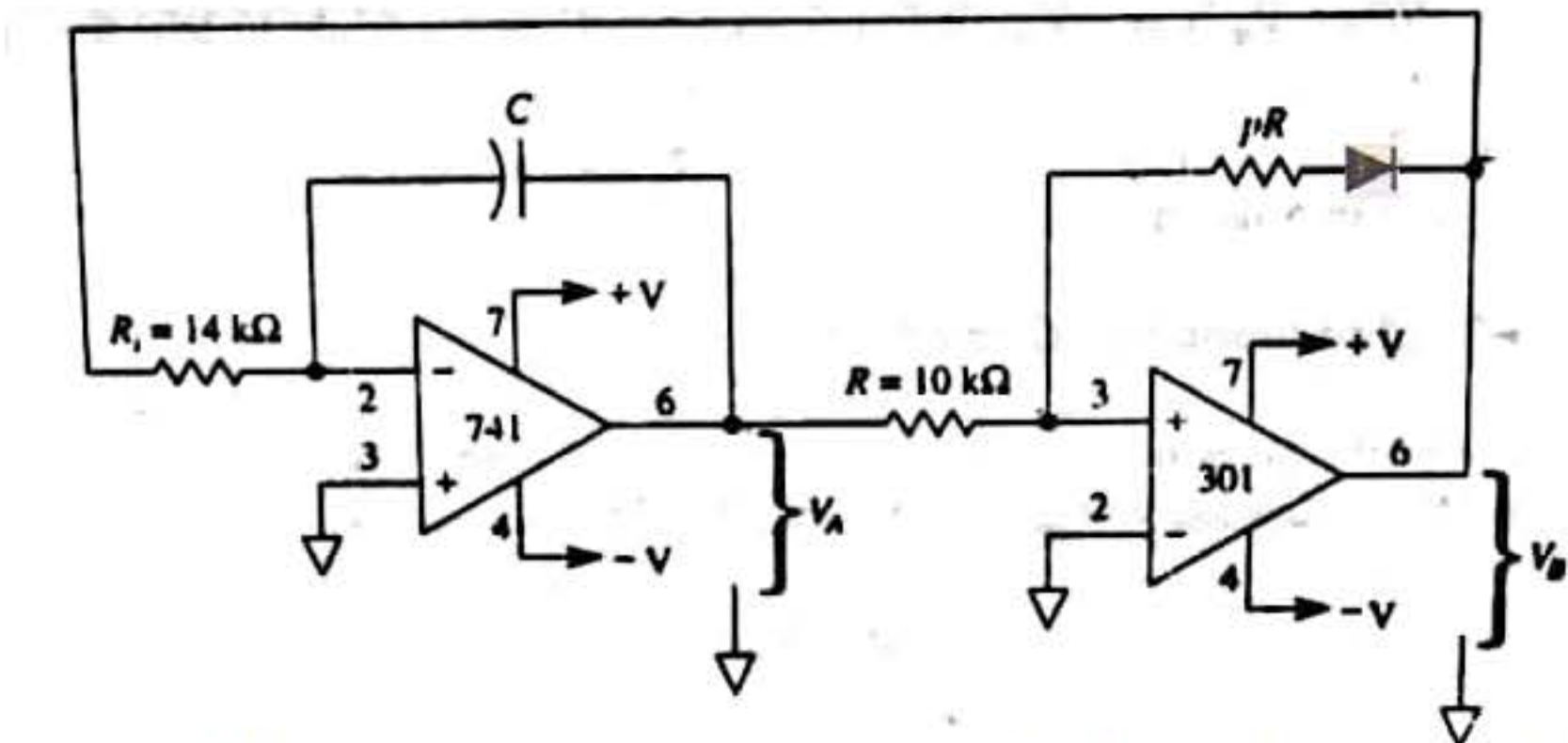

We updated the previous circuit (HW 8.2.1) by placing a diode  $V_D$  (conducting)  $= 0.6\text{V}$  right after the  $pR$  resistor.

Find the approximate peak value of the voltage  $V_{UT}$  in  $\text{V}$ .

✓

4.7826

Find the new frequency  $f$  in  $\text{kHz}$ .

✓

1

Save Show answer





## Homework 8.3

Homework due Sep 2, 2022 23:59 +06 Completed

[Bookmark this page](#)

### HW 8.3.1

10.0/10.0 points (graded)

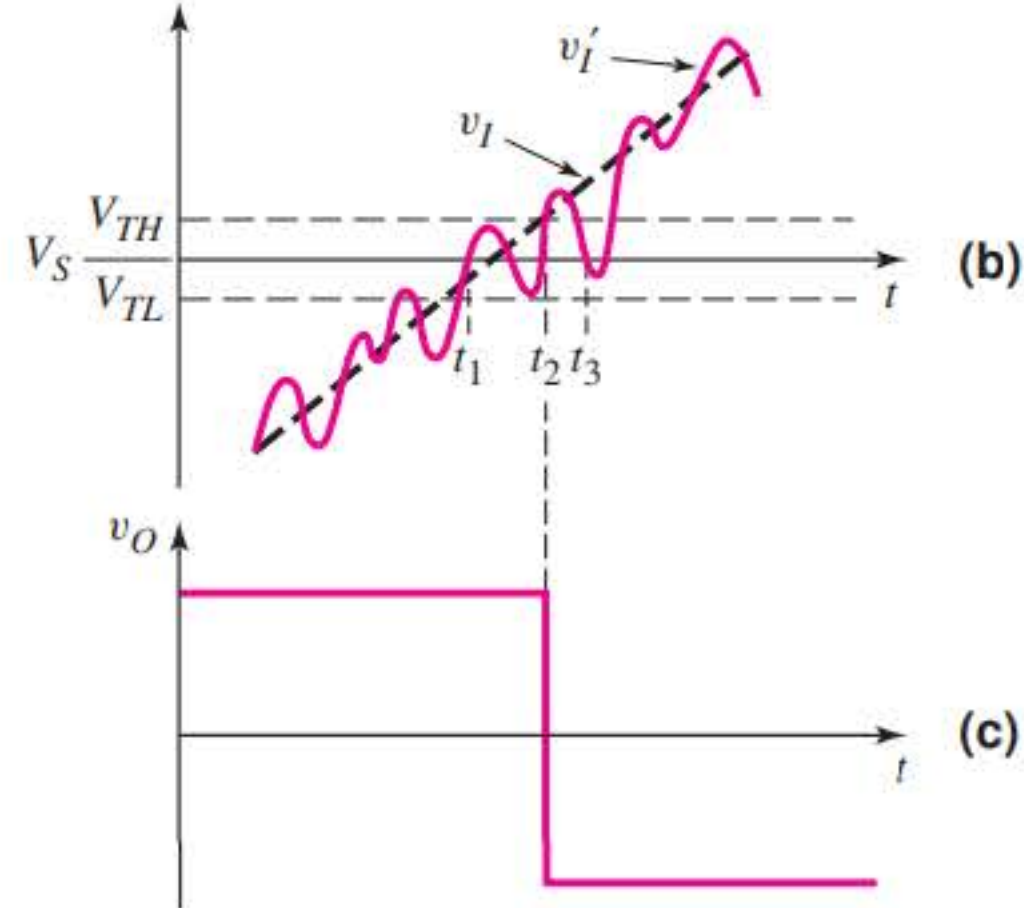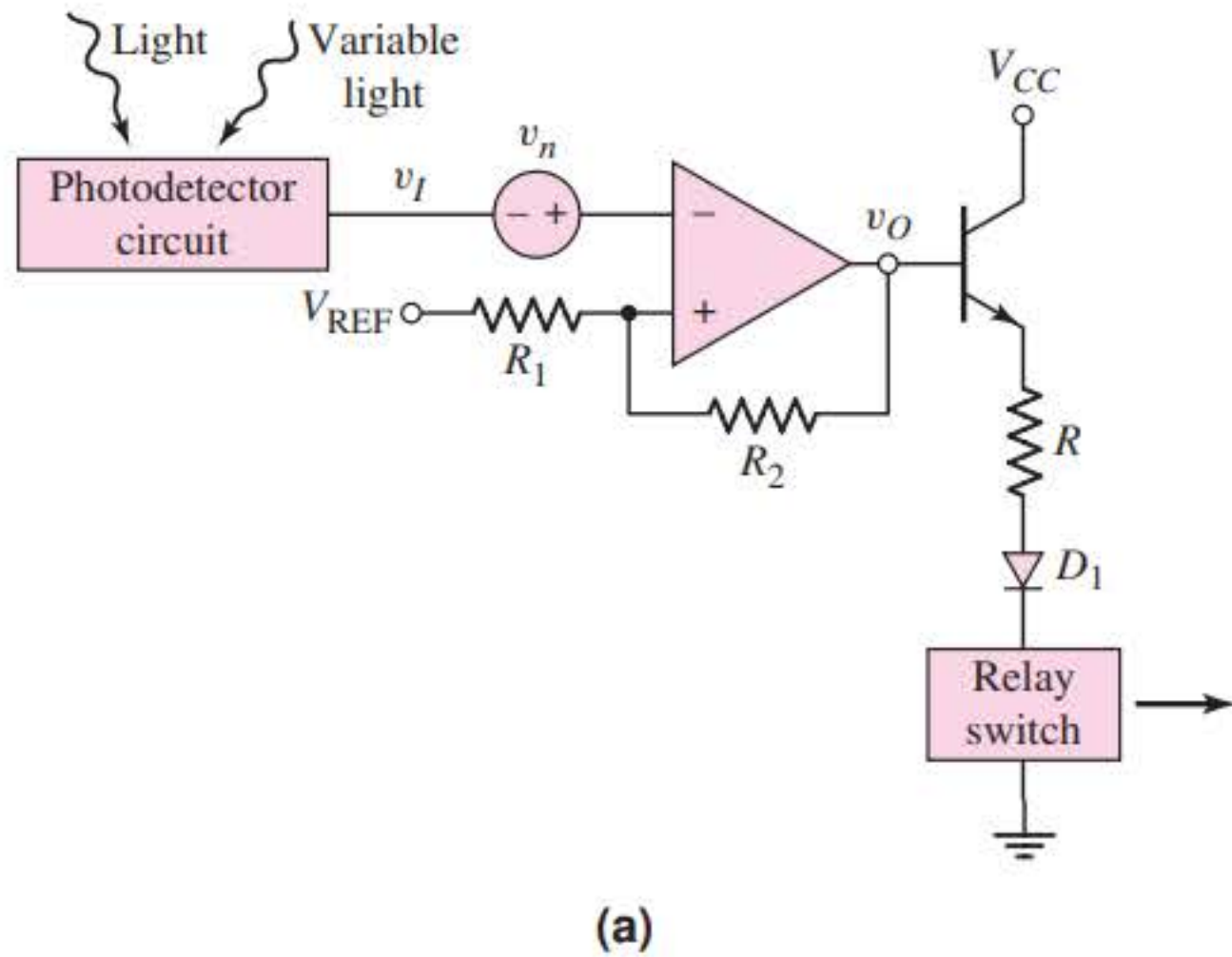

Here assume conduction voltage of diode is  $V_\gamma = 0.7V$  and for the switching transistor  $V_{BE}(on) = 0.7V$  and  $\beta_F$  is very large.

Design the street light control circuit shown in the above figure such that the switching voltage is  $V_S = 2V$  and the hysteresis width is  $200mV$ . Assume  $V_H = 10V$  and  $V_L = -6V$ .

Find the resistances in  $k\Omega$ . You can assume the value of one resistance.

$R_1$

1



$R_2$

79



Find the value of  $V_{REF}$  in  $V$ .

2.025316



2.025316

Suppose, the current through resistance  $R$  is  $150\mu A$  when  $v_O = V_H$  and relay switch resistance is  $330\Omega$ .

Find the value of  $R$  in  $k\Omega$ .

57.0033



57.0033

Save


## Homework 8.4

Homework due Sep 2, 2022 23:59 +06 Completed

[Bookmark this page](#)

### HW 8.4.1

24.0/24.0 points (graded)

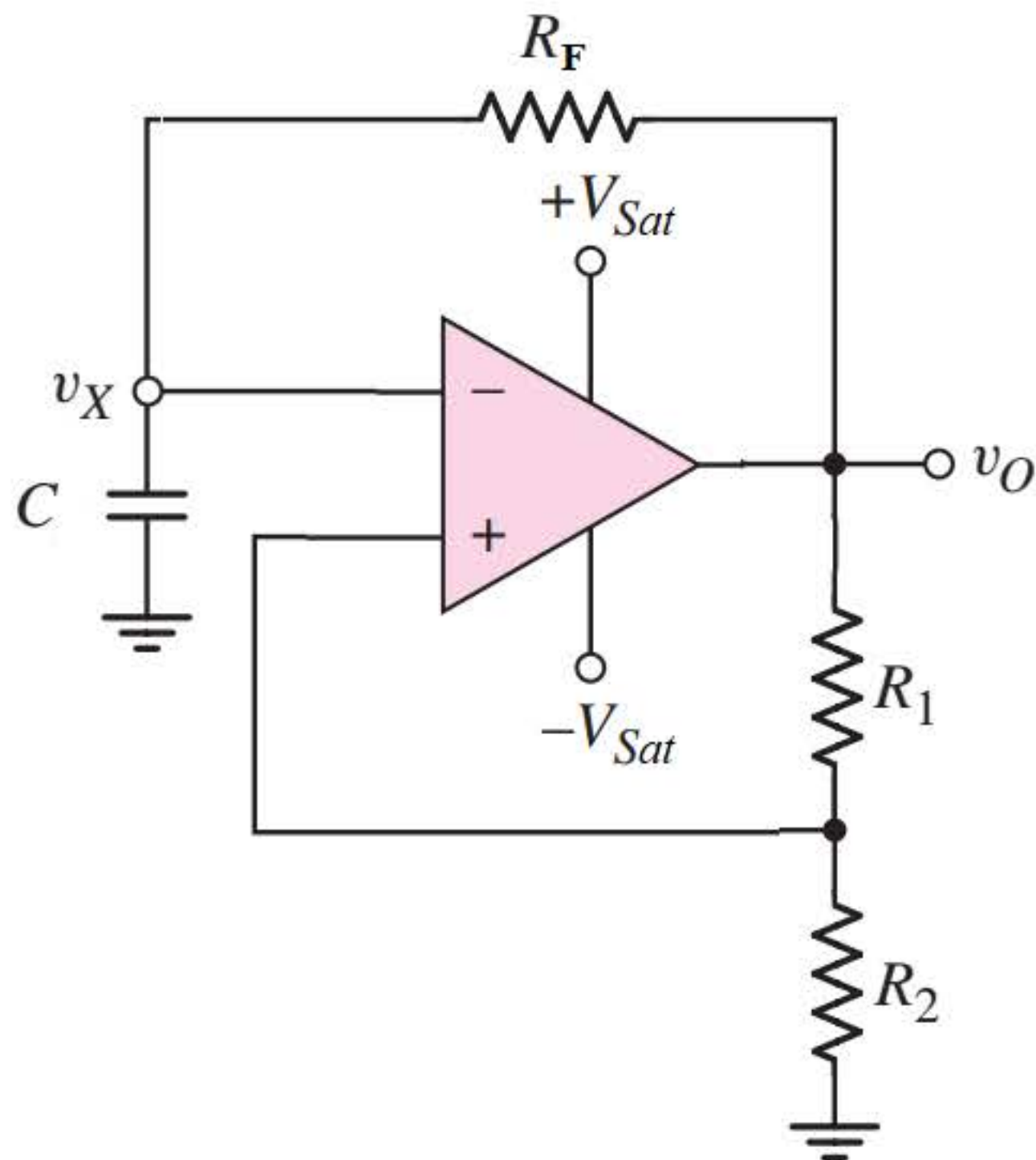

Design a square wave generator such that it has frequency  $4kHz$  and duty cycle  $30\%$ .

Find the resistances in  $k\Omega$ , capacitance in  $\mu F$ , voltage in  $V$ . Use minus sign while submitting the value of  $-V_{Sat}$ , it may or may not have same absolute value of  $+V_{Sat}$ . You can assume any value if needed.

$R_1$

1



$R_2$

0.26



$C$

0.01



$R_F$

25



$+V_{Sat}$

1



$-V_{Sat}$

-0.345



8.1

Upper threshold voltage.

$$V_{TU} = +V_{sat} \times \frac{R_2}{R_1 + R_2}$$
$$= 20 \times \frac{172}{372} = 9.2473 \text{ V}$$

Lower threshold voltage.

$$V_{TL} = -V_{sat} \times \frac{R_2}{R_1 + R_2}$$
$$= -20 \times \frac{172}{372} = -9.2473 \text{ V}$$

$$T_1 = C \ln \left( \frac{(+V_{sat}) - V_{TL}}{(+V_{sat}) - V_{TU}} \right)$$

$$= R_f C \ln \left( \frac{(+V_{sat}) - V_{TL}}{(+V_{sat}) - V_{TU}} \right)$$

$$= 10 \text{ ms} \times \ln \left( \frac{20 + 9.2473}{20 - 9.2473} \right) = 10.006 \text{ ms}$$

$$T_2 = \tau \ln \left( \frac{(-V_{sat}) - V_{T_U}}{(-V_{sat}) - V_{T_L}} \right)$$

$$= R_f C \ln \left( \frac{(-V_{sat}) - V_{T_U}}{(-V_{sat}) - V_{T_2}} \right)$$

$$= 10 \text{ ms} \times \ln \left( \frac{-20 - 9.2473}{-20 + 9.2473} \right)$$

$$= 10.006 \text{ ms}$$

$$\therefore \text{Total time} = t_1 + t_2 = 20.0126 \text{ ms}$$



8.2.1

$$f = 500 \text{ Hz} = 0.5 \text{ kHz}$$

$$T = \frac{1}{f} = \frac{1}{0.5} = 2 \text{ ms}; V_{UT} \approx 5 \text{ V}$$

$$V_{UT} = -\left(\frac{-V_{\text{sat}}}{P}\right) = -\left(\frac{-13.8}{P}\right)$$

$$\Rightarrow P = \frac{13.8}{5} = 2.76$$

$$\therefore PR = 2.76 \times 10 = \boxed{27.6 \text{ k}\Omega}$$

$$f = \frac{P}{4R_i C} = \frac{2.76}{4 \times 14 \times C}$$

$$\Rightarrow C = \frac{2.76}{4 \times 14 \times 500} = \boxed{0.1 \mu\text{F}}$$

8.2.2

$$V_{UT} \approx - \left( \frac{-V_{sat} + 0.6}{\rho} \right)$$
$$= \frac{13.2}{2.76} = 4.7826 \text{ V}$$

$$\text{new frequency} = 0.5 \times 2$$
$$= 1 \text{ kHz}$$



8.3.1

$$\text{hysteresis width} = V_{TH} - V_{TL}$$

$$= \left( V_H \times \frac{R_1}{R_1 + R_2} \right) - \left( V_L \times \frac{R_1}{R_1 + R_2} \right)$$

$$\Rightarrow 200 \times 10^{-3} = (V_H - V_L) \times \frac{R_1}{R_1 + R_2}$$

$$\Rightarrow 200 \times 10^{-3} = (10 + 6) \times \frac{1}{1 + \frac{R_2}{R_1}}$$

$$\Rightarrow \frac{R_2}{R_1} = \frac{16}{200 \times 10^{-3}} - 1 = 80 - 1 = 79$$

$$\boxed{R_1 = 1 \text{ k}\Omega} \quad \boxed{R_2 = 79 \text{ k}\Omega}$$

$$V_{ref} = V_s \times \frac{R_1 + R_2}{R_2} = 2 \times 1.01265 \text{ V}$$

$$\boxed{= 2.025316 \text{ V}}$$

$$V_x = 150 \times 10^{-6} \times 330 = 0.0495 \text{ V}$$

$$V_y = V_x + 0.7 = 0.7495 \text{ V}$$

$$R = \frac{V_H - V_{y-0.7}}{150 \times 10^{-6}} = \frac{10 - 0.7495 - 0.7}{150 \times 10^{-6}}$$

$$= 57.0033 \text{ k}\Omega$$

8.4.1

$$\text{frequency} = 4 \text{ kHz}$$

$$\therefore T = \frac{1}{f} = \frac{1}{4 \times 10^3} = 0.25 \text{ ms}$$

$$\text{duty cycle} = 30\%$$

$$\therefore T_1 = (30\%) \times T = \frac{30}{100} \times 0.25 \\ = 0.075 \text{ ms}$$

$$\therefore T_2 = T - T_1 = 0.25 - 0.075 = 0.175 \text{ ms}$$

Assume that,  
 $\tau = \tau = 0.25 \text{ ms}$ ,  $C = 0.01 \mu\text{F}$ ,  $R_F = 25 \text{ k}\Omega$

$$\therefore \tau_c = \tau \ln \left( \frac{V_H - V_{L+}}{V_H - V_{UT}} \right)$$

$$= \tau \ln \left( \frac{V_H - V_L \left( \frac{R_2}{R_1 + R_2} \right)}{V_H - V_H \left( \frac{R_2}{R_1 + R_2} \right)} \right)$$

$$\Rightarrow e^{\frac{\tau_c}{\tau}} = \frac{V_H - \frac{V_L R_2}{R_1 + R_2}}{V_H \left( 1 - \frac{R_2}{R_1 + R_2} \right)}$$

$$\Rightarrow e^{\frac{\tau_c}{\tau}} = \frac{V_H - \frac{V_L R_2}{R_1 + R_2}}{\frac{V_H R_1}{R_1 + R_2}}$$

$$\Rightarrow e^{\frac{\tau_c}{\tau}} = \frac{R_1 + R_2}{R_1} - \frac{V_L R_2}{V_H R_1}$$

$$\Rightarrow e^{\frac{0.075}{0.25}} = \left( 1 + \frac{R_2}{R_1} \right) - \frac{V_L}{V_H} \left( \frac{R_2}{R_1} \right)$$

$$\Rightarrow e^{0.3} = (1 + x) - xy \quad \text{--- (i)}$$

$$\therefore T_2 = T \ln \left( \frac{V_L - V_{UT}}{V_L - V_{LT}} \right)$$

$$\Rightarrow e^{\frac{T_2}{T}} = \frac{R_1 + R_2}{R_1} - \frac{V_H}{V_L} \frac{R_2}{R_1}$$

$$\Rightarrow e^{\frac{0.175}{0.25}} = \left( 1 + \frac{R_2}{R_1} \right) - \frac{1}{\frac{V_L}{V_H}} \times \frac{R_2}{R_1}$$

$$\Rightarrow e^{0.7} = (1+x) - \left( \frac{x}{y} \right) \text{ --- (1)}$$

$$\textcircled{i} \Rightarrow$$

$$e^{0.3} = (1+x) - xy$$

$$\therefore y = \frac{1+x - e^{0.3}}{x}$$

$$\textcircled{ii} \Rightarrow$$

$$e^{0.7} = (1+x) - \left( \frac{x}{\frac{1+x - e^{0.3}}{x}} \right)$$

$$\Rightarrow e^{0.7} = (1+x) - \frac{x^2}{1+x - e^{0.3}}$$



$$\therefore x = 0.26$$

$$\therefore y = \frac{1 + 0.26 - e^{0.3}}{0.26} = -0.3456$$

$$\therefore \frac{R_2}{R_1} = x \Rightarrow \frac{R_2}{R_1} = 0.26$$

$$\therefore \frac{V_L}{V_H} = y \Rightarrow \frac{V_L}{V_H} = -0.3456$$

$$\therefore R_1 = \boxed{1 \text{ k}\Omega} \quad R_2 = \boxed{0.26 \text{ k}\Omega}$$

$$\boxed{+V_{\text{sat}} = 1 \text{ V}} , \quad \boxed{-V_{\text{sat}} = -0.345 \text{ V}}$$