


Homework 6.1

Homework due Aug 24, 2022 23:59 +06 Completed

[Bookmark this page](#)

HW 6.1.1

5.0/5.0 points (graded)

 

In the above **PMOS inverter circuit** $V_{DD} = 5V$ and $R_D = 20k\Omega$

For p-channel MOSFET conduction parameter $K_p = 0.3mA/V^2$ and threshold voltage $V_{TP} = -0.5V$

If the input voltage $v_I = 5V$.

Find the ouput voltage v_O in V .

✓

0

Find the drain current i_D in mA

✓

0

Submit You have used 1 of 4 attempts

HW 6.1.2

5.0/5.0 points (graded)

If the input voltage $v_I = 1V$.

Find the ouput voltage v_O in V .

✓

4.882

Find the drain current i_D in mA


✓

0.2441

Submit You have used 2 of 5 attempts

HW 6.1.3

5.0/5.0 points (graded)

 

In the above circuit $V_{DD} = 5V$ and for n-channel MOSFET threshold voltage $V_{TN} = 1V$, conduction parameter $K_n = 10\mu A/V^2$

If the transition input voltage is $v_I = 2V$, find out the value of R_D in $k\Omega$?


✓

400

Submit You have used 1 of 5 attempts

HW 6.1.4

5.0/5.0 points (graded)

 

In the above NMOS NOR gate circuit $R_D = 1k\Omega$ and for both n-channel MOSFETs conduction parameter $K_n = 2mA/V^2$, threshold voltage $V_{TN} = 0.5V$.

Remember that voltage swing for both inputs V_1, V_2 are in between $0V$ to $2.5V$.

Find the maximum power dissipation in mW .

✓

5.8686675

In this case, find the output voltage V_O in V .

✓

0.152533


Submit You have used 1 of 5 attempts

Homework 6.2

Homework due Aug 24, 2022 23:59 +06 Completed
[Bookmark this page](#)

HW 6.2.1

5.0/5.0 points (graded)

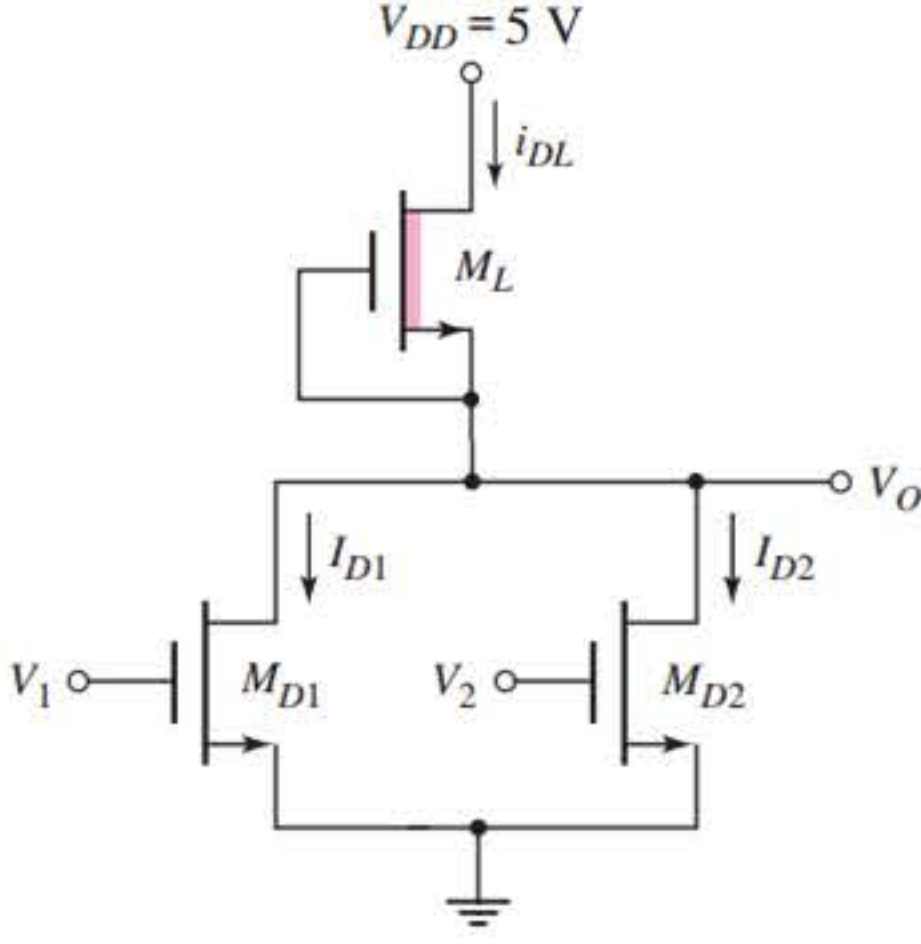

In the above circuit $V_{DD} = 5V$.

The **process conduction parameter** for all three MOSFETs is $k'_n = 2mA/V^2$.

The aspect ratio for the n-channel depletion type MOSFET M_L is $(W/L)_L = 1$.

The threshold voltage for the n-channel depletion type MOSFET M_L is $V_{TNL} = -0.6V$.

The aspect ratio for the n-channel enhancement type MOSFET M_{D1} is $(W/L)_{D1} = 4$.

The aspect ratio for the n-channel enhancement type MOSFET M_{D2} is $(W/L)_{D2} = 2$.

The threshold voltage of the both n-channel enhancement type MOSFET M_{D1} and M_{D12} is $V_{TND} = 0.4V$.

Let $V_1 = 5V$ and $V_2 = 0V$.

Find the output voltage v_O in mV .

✓

9.7930

Find the current i_{DL} in mA .

✓

0.72

Find the current i_{D1} in mA .

✓

0.72

Find the current i_{D2} in mA .

✓

0

Find the power dissipation in mW .

✓

3.6

Submit

You have used 1 of 5 attempts

HW 6.2.2

5.0/5.0 points (graded)

Let $V_1 = 0V$ and $V_2 = 5V$.

Find the output voltage v_O in mV .

✓

19.607

Find the current i_{DL} in mA .

✓

0.72

Find the current i_{D1} in mA .

✓

0

Find the current i_{D2} in mA .

✓

0.72

Find the power dissipation in mW .

✓

3.6

Submit

You have used 3 of 5 attempts

HW 6.2.3

5.0/5.0 points (graded)

Let $V_1 = 5V$ and $V_2 = 5V$.

Find the output voltage v_O in mV .

✓

6.5263688

Find the current i_{DL} in mA .

✓

0.72

Find the current i_{D1} in mA .

✓

0.4799

Find the current i_{D2} in mA .

✓

0.2399

Find the power dissipation in mW .

✓

3.6

Submit

You have used 1 of 5 attempts


Homework 6.3

Homework due Aug 24, 2022 23:59 +06 Completed


Bookmark this page

HW 6.3.1

8.0/8.0 points (graded)

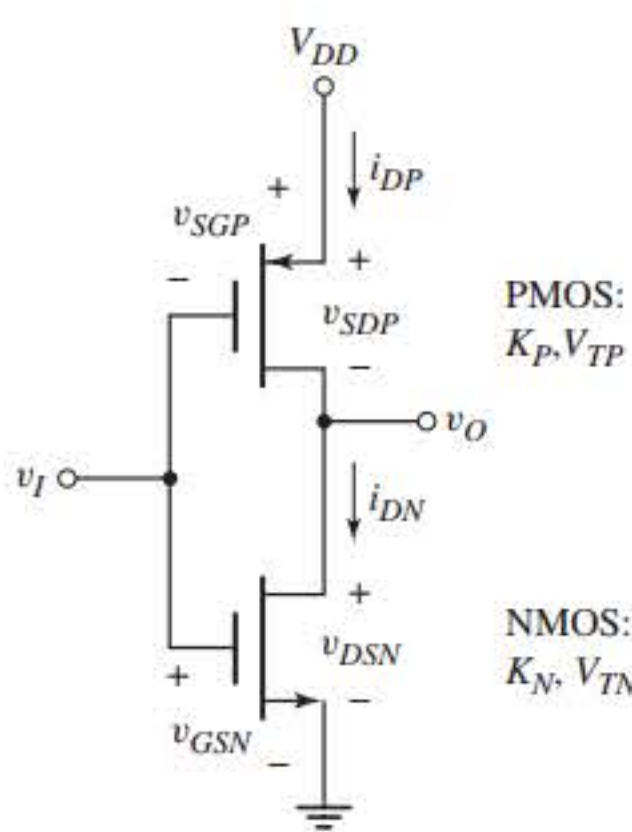

 In the circuit above CMOS inverter is biased at $V_{DD} = 1.8V$. The transistor parameters are $V_{TN} = -V_{TP} = 0.4V$ and $K_n/K_p = 5/2$.



Find the value of V_{IH} in V .

0.876657

✓

0.876657

Find the value of V_{OLU} in V .

0.1336599

✓

0.1336599

Find the value of V_{IL} in V .

0.632266

✓

0.632266

Find the value of V_{OHU} in V .

1.7064655

✓

1.7064655

Find the value of NM_L in V .

0.632266-0.1336599

✓

0.632266 – 0.1336599

Find the value of NM_H in V .

1.7064655-0.876657

✓

1.7064655 – 0.876657

Find the value of Noise Margin in V .

0.632266-0.1336599

✓

0.632266 – 0.1336599


Save

Submit

You have used 6 of 14 attempts

HW 6.3.2

6.0/6.0 points (graded)

 

In this transfer characteristics curve V_{OPt} represents the transition output voltage for PMOS and V_{ONt} represents the transition output voltage for NMOS and V_{It} represents the transition input voltage.

Find the value of V_{It} for the circuit in V . **Hint:** remember that $V_{DS} = V_{GS} - V_{TN}$ for NMOS is at the transition point or $V_{SD} = V_{SG} + V_{TP}$ for PMOS is at the transition point. Moreover, in the picture while the transistors are in between transition points input voltage is equal to V_{It} .

0.7874258867

✓

0.7874258867

Find the value of V_{OPt} for the circuit in V .

1.187425

✓

1.187425

Find the value of V_{ONt} for the circuit in V .

0.387425

✓

0.387425


Homework 6.4

Homework due Aug 24, 2022 23:59 +06 Completed

Bookmark this page

HW 6.4.1

6.0/6.0 points (graded)

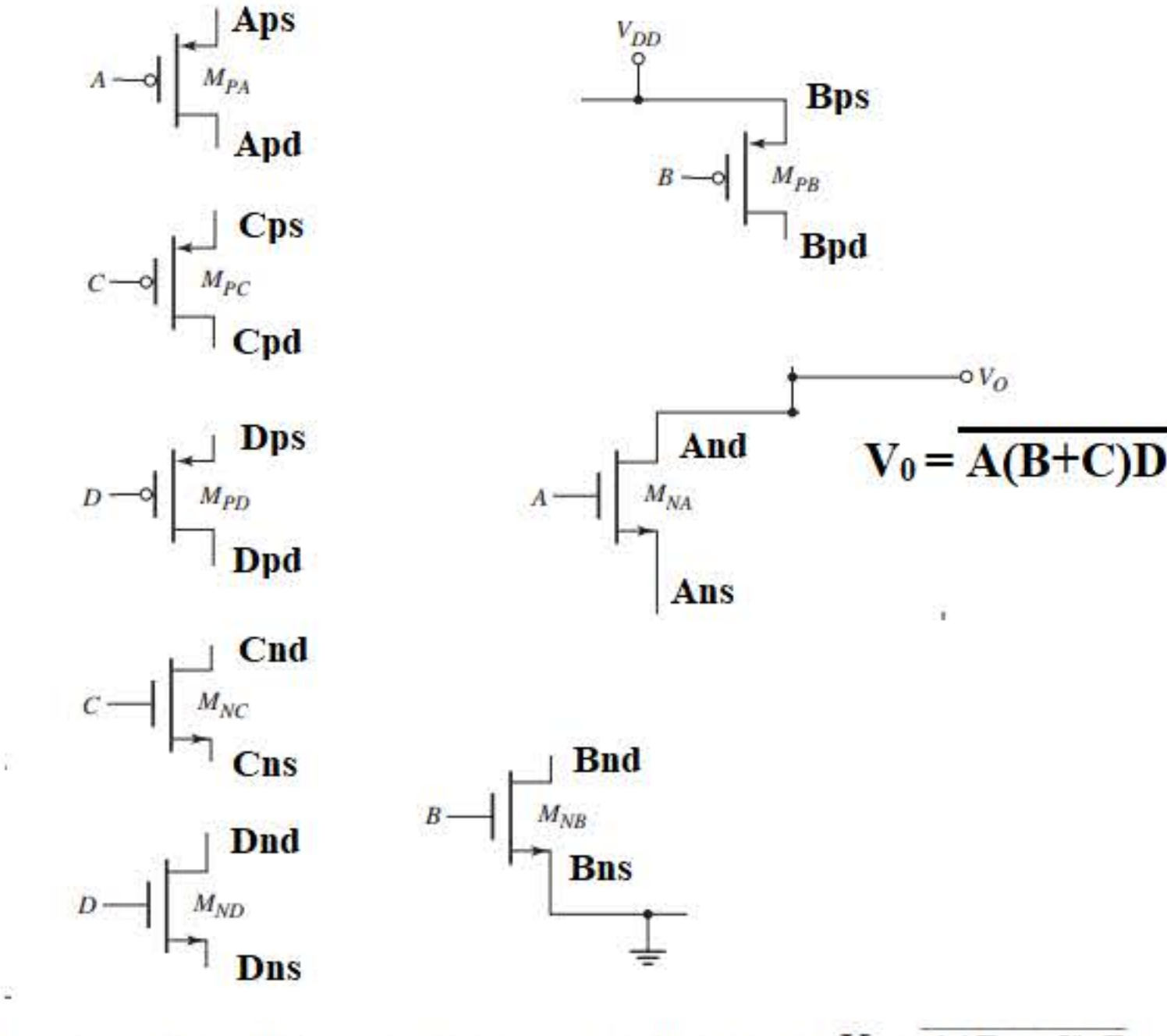

This is the CMOS logic implementation of logic equation $Y = A(B + C)D$. Some of the connections are already given and you need to provide the rest of the correct connection for this circuit.

Select all the terminal(s) that must be connected to the node *Bnd*.

☐ Dnd

☒ Dns

☒ Cnd

☐ Cns

☐ Ans

☐ Cpd

☐ Cps



Select all the terminal(s) that must be connected to the node *Bns*.

☐ Dnd

☐ Dns

☐ Cnd

☒ Cns

☐ Ans

☐ Cpd

☐ Cps



Select all the terminal(s) that must be connected to the node *Ans*.

☒ Dnd

☐ Dns

☐ Cnd

☐ Cns

☐ Bnd

☐ Cpd

☐ Cps



Select all the terminal(s) that must be connected to the node *And*.

☒ Dpd

☐ Dps

☒ Cpd

☐ Cps

☐ Bps

☐ Bpd

☒ Apd

☐ Aps



Select all the terminal(s) that must be connected to the node *Bpd*.

☐ Dpd

☐ Dps

☐ Cpd

☒ Cps

☐ Bps

☐ Bpd

☐ Apd

☐ Aps



Select all the terminal(s) that must be connected to the node *Bps*.

☐ Dpd

☒ Dps

☐ Cpd

☐ Cps

☐ Bps

☐ Bpd

☐ Apd

☒ Aps




Save

Submit You have used 2 of 8 attempts

HW 6.4.2

4.0/4.0 points (graded)

 

Q_a , Q_b and Q_c are the outputs of three differenet sequential circuits with D as data input and $Clock$ as ϕ signal.

Select the correct answer(s) by examining the timing diagram displayed above.

☒ Q_a is the output of a positive level D-latch and Q_b is the output of a positive edge-triggered D-flip flop.

☐ Q_a is the output of a negative level D-latch and Q_b is the output of a positive edge-triggered D-flip flop.

☐ Q_a is the output of a positive level D-latch and Q_b is the output of a negative edge-triggered D-flip flop.

☐ Q_b is the output of a positive edge-triggered D-flip flop and Q_c is the output of a positive edge-triggered D-flip flop.

☒ Q_b is the output of a positive edge-triggered D-flip flop and Q_c is the output of a negative edge-triggered D-flip flop.

☐ Q_b is the output of a negative edge-triggered D-flip flop and Q_c is the output of a positive edge-triggered D-flip flop.

☐ Q_a is the output of a positive level D-latch and Q_c is the output of a positive edge-triggered D-flip flop.

☐ Q_a is the output of a negative level D-latch and Q_c is the output of a positive edge-triggered D-flip flop.

☒ Q_a is the output of a positive level D-latch and Q_c is the output of a negative edge-triggered D-flip flop.



Save