

Table 2: NAND Gate Data

$V_A$ (V)	$V_B$ (V)	$V_{DA}$ (V)	$V_{DB}$ (V)	$V_P$ (V)	$I_{R1}$ (mA)	$I_{R2}$ (mA)	$V_B$ (mV)	$V_Y$ (V)
4.95	4.95	-3.11	-3.11	1.81	1.42	2.28	1.71	0.02
4.95	0	-4.43	0.5	0.5	2.01	0.03	0.01	4.93
0	0	0.49	0.49	0.5	2.01	0.032	0.01	4.93
0	4.95	0.60	-4.33	0.6	1.96	0.027	0.03	4.94

Table 3: Inverter Data

Input A (V)	Input B (V)	$V_P$ (V)	$V_B$ (V)	Output Y (V)
4.95	0	0.5	0.01	4.93
4.95	4.95	1.81	0.71	0.02



Signature

## Report

Please answer the following questions briefly in the given space.

1. Using experimental data, find the operating mode of **Q1** when input **A** is **HIGH** and input **B** is **LOW**. Additionally, find whether diodes **DA** and **DB** are **ON** or **OFF** (by using the voltage across them).

Ans.

Here,  $I_E = 0 \text{ mA}$

$$I_B = \frac{V_B - 0}{19.45} = 0.01 \approx 0 \text{ mA}$$


$$I_E = I_{R_2} = 0.03 \approx 0 \text{ mA}$$

$\therefore Q_1$  is in cutoff mode

for Diode  $D_A$ ;

Voltage in cathode > voltage in anode  
which means  $D_A$  is off

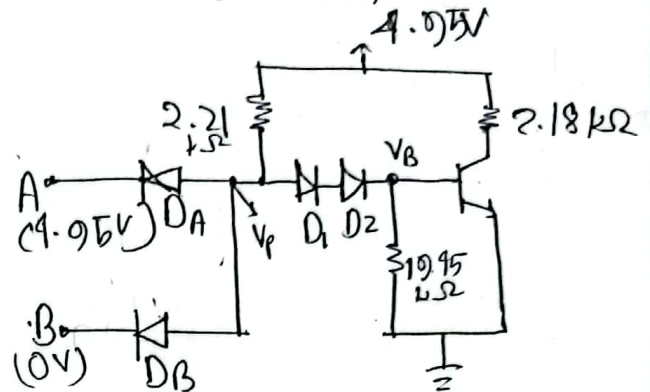
for  $D_B$ , voltage in cathode < Voltage in anode, meaning  
 $D_B$  is ON.



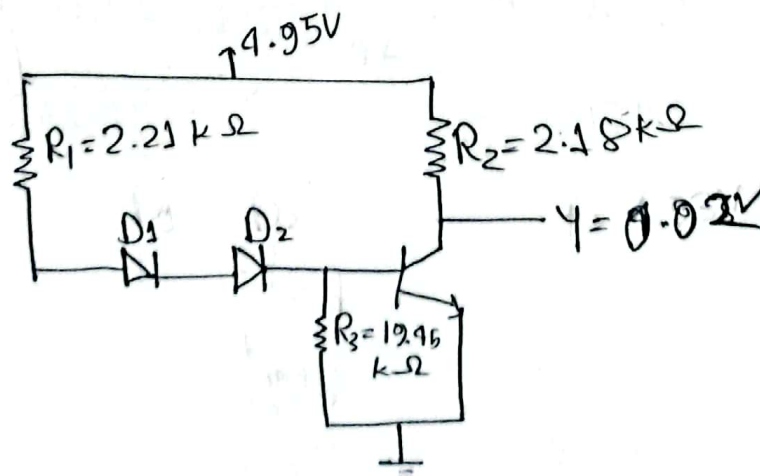2. Assume that the output of the circuit shown in Fig: 1 is **LOW**. Draw the partial circuit consisting of only those components which remain active.

Ans.

In order to get Low output from this circuit, diodes  $D_A$  and  $D_B$  have to be off. Therefore the active part of the circuit is drawn below:



3. What should be the relation between the currents  $I_{R1}$ ,  $I_B$  and  $I_{RB}$  when all inputs are HIGH? Did you obtain a similar result in your experiment? Explain briefly. (use a Multi-meter as Ammeter to measure  $I_B$ ).

Ans. When all inputs are HIGH, diodes DA and DB are OFF while D1 and D2 are ON.  $I_{R1}$  can travel through D1 and D2 and be divided into  $I_B$  and  $I_{RB}$

$$\text{theoretically } I_{RB} = \frac{V_B - 0}{20k\Omega} = \frac{0.7 - 0}{20k\Omega} = 0.035 \text{ mA}$$

$$\therefore I_B = I_{R1} - I_{RB} = 1.42 - 0.035 = 1.385 \text{ mA}$$

$$\text{from the experiment, we get } I_{RB}^* = \frac{0.71 - 0}{10.45} \text{ mA} = 0.037 \text{ mA}$$

$$\therefore \text{Experimentally } I_B = I_{R1} - I_{RB}^* = 1.383 \text{ mA}$$

$\therefore$  Theoretical  $I_B$  is very close to experimental  $I_B$   
Because the  $I_{R1} = I_{RB} + I_B$  relation is True.

4. Use the relation between the currents  $I_{R1}$ ,  $I_B$  and  $I_{RB}$  when all inputs are HIGH to verify the operating mode of Q1. [Assume beta ( $\beta_F$ )  $\geq 100$ ]

Ans.

The experimental value of  $y$  when both of the inputs are high is 0.02V. This suggests Q1 is in saturation mode.

$$\text{Here, } I_E = I_{R2} = 2.28 \text{ mA}$$

$$I_B = 1.383 \text{ mA} \quad \frac{I_E}{I_B} = \frac{2.28}{1.383} = 1.64 < \beta_F$$

which verifies that Q1 is in saturation

5. Will the circuit still work properly as NAND gate if the diodes  $D_1$  and  $D_2$  are removed? Measure the output voltage for the four different cases and verify.

Ans.

$V_A$	$V_B$	$V_Y$
0	0	4.94
0	4.95	4.95
4.95	0	4.94
4.95	4.95	0.03


6. Vary the input A from 0V to 5V while keeping input B fixed at 5V. What is the maximum value of input A for which the output remains HIGH? [consider any voltage above 1V as HIGH]

Ans.

1.08 V. is the maximum value of input A  
for which the output remains HIGH



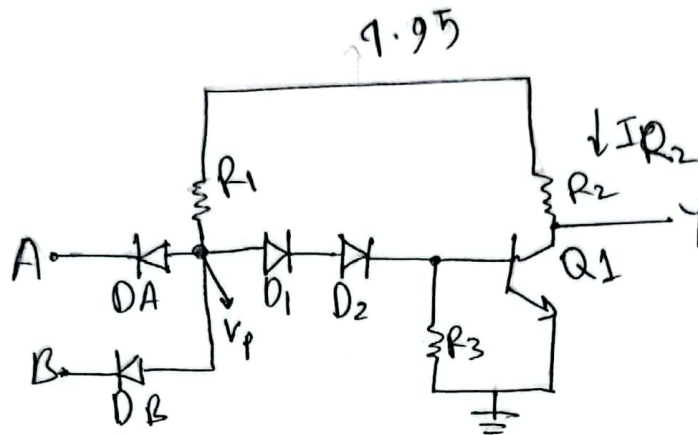7. Verify the result of table 2 using theoretical calculation and comment on the result (Use extra paper necessary).



1

theoretically, when A and B are both high (9.95V), DA and DB should be OFF and  $V_p$  will be High, resulting in the transistor to be in saturation mode. Therefore, output should be Low,  $V_B$  should be near 0.7 and  $I_e > 0$ . All of these assumptions are proven true in the first row of Data Table 2.

When either of the inputs are low,  $V_p$  remains Low resulting in the transistor to be in cutoff mode and the output to be High.  $I_e$ ,  $I_B$  and  $I_B$  should be near zero. These assumptions are also proven right in the 2nd and 9th row of Data Table 2.

finally if both of the inputs are low, that would result in DA, DB ON,  $V_p = \text{Low}$ , Q1 is in saturation, output is High. Also proven right in row 3 of the table.