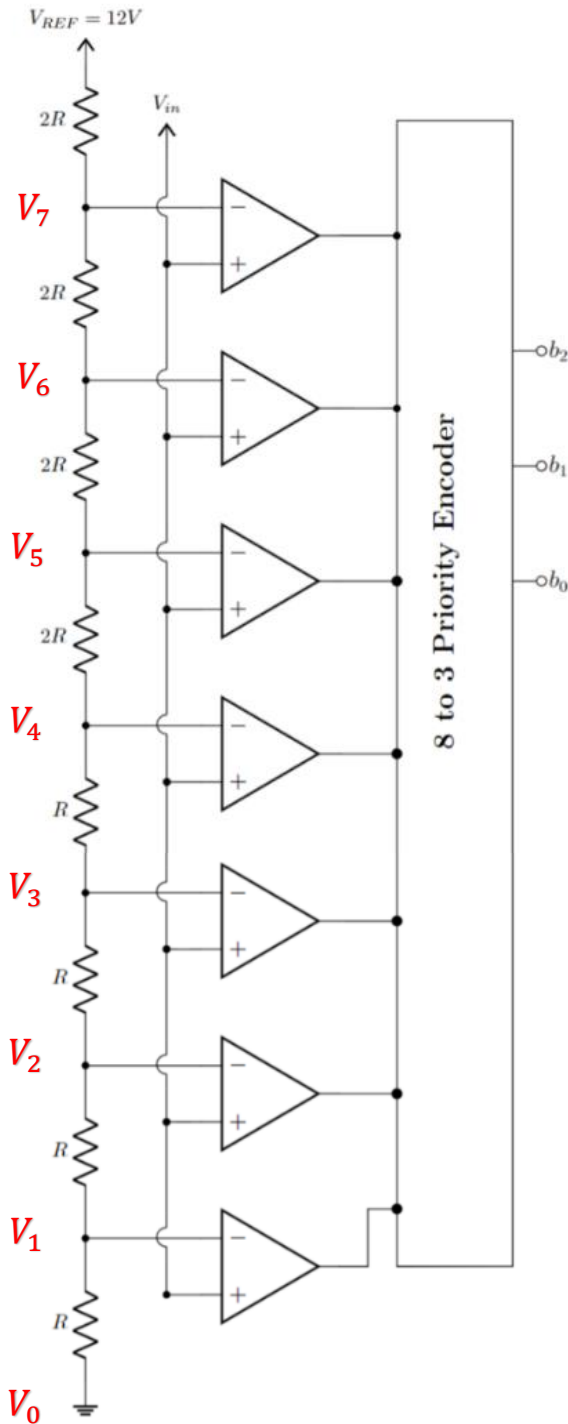


## ADC (non-uniform)

Q1 For the shown 3-bit Flash ADC in the figure, **draw** the '*V<sub>in</sub>-vs-Digital Output*' staircase plot. If a current of 0.303mA is flowing through the resistors, **find** the value of  $R$ . [ $V_{REF} = 12V$ ]




$$I = \frac{V_{REF}}{12R}$$


$$\Rightarrow 0.303 = \frac{12}{12R}$$

$$\therefore R = 3.3 \text{ k}\Omega$$


$V_0 = 0V$	000
$V_1 = I \times R = 1V$	001
$V_2 = I \times 2R = 2V$	010
$V_3 = I \times 3R = 3V$	011
$V_4 = I \times 4R = 4V$	100
$V_5 = I \times 6R = 6V$	101
$V_6 = I \times 8R = 8V$	110
$V_7 = I \times 10R = 10V$	111
$V_8 = V_{REF} = 12V$	

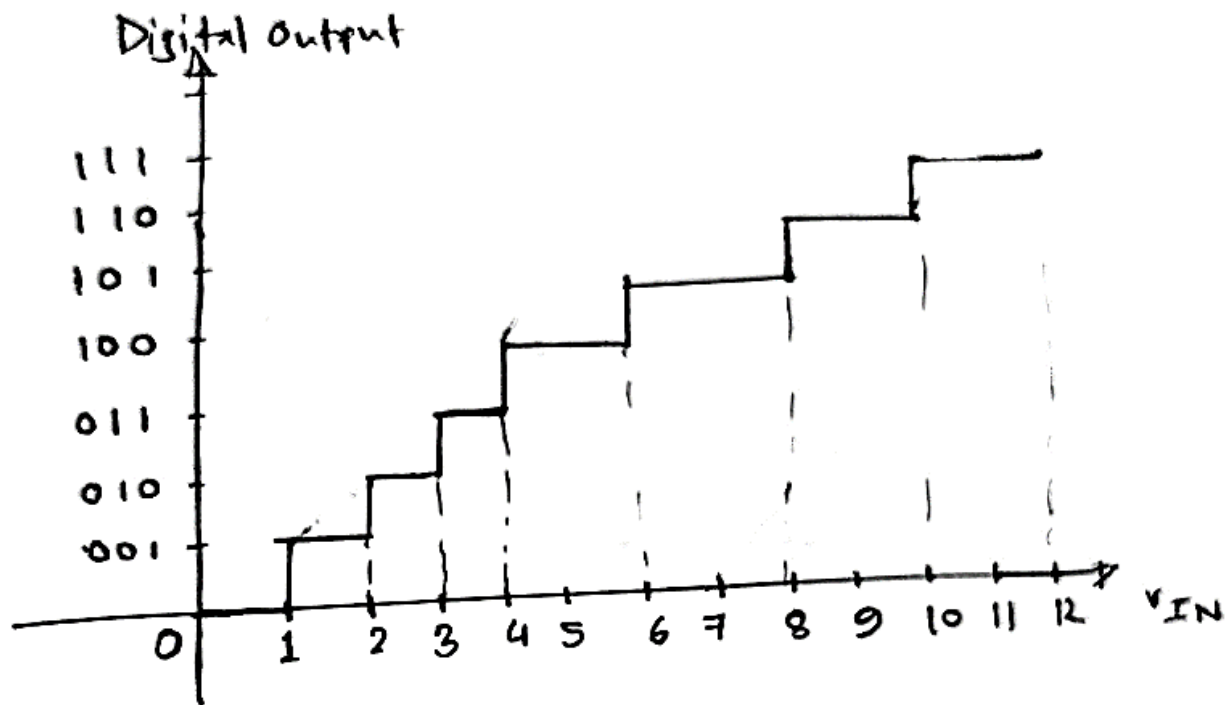

Q2	Design a Flash ADC using the transfer curve below.
----	--

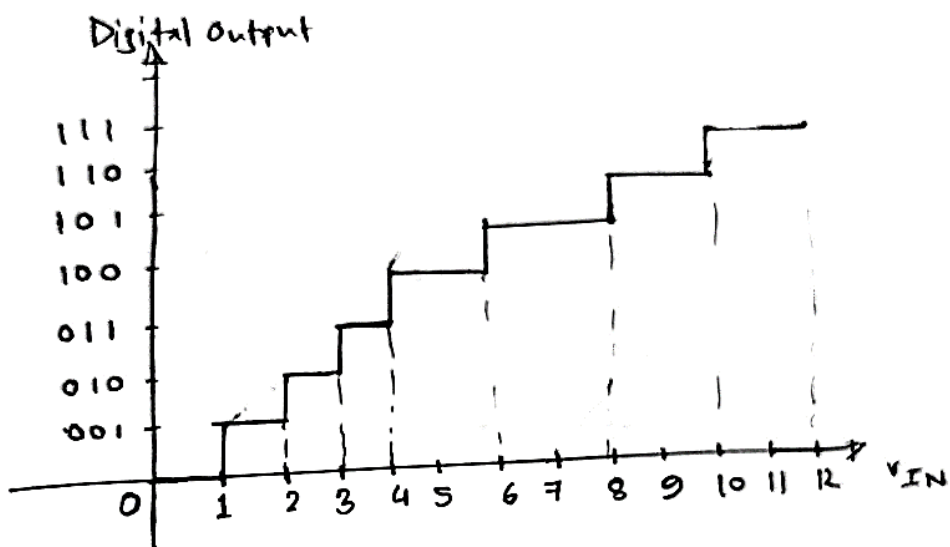

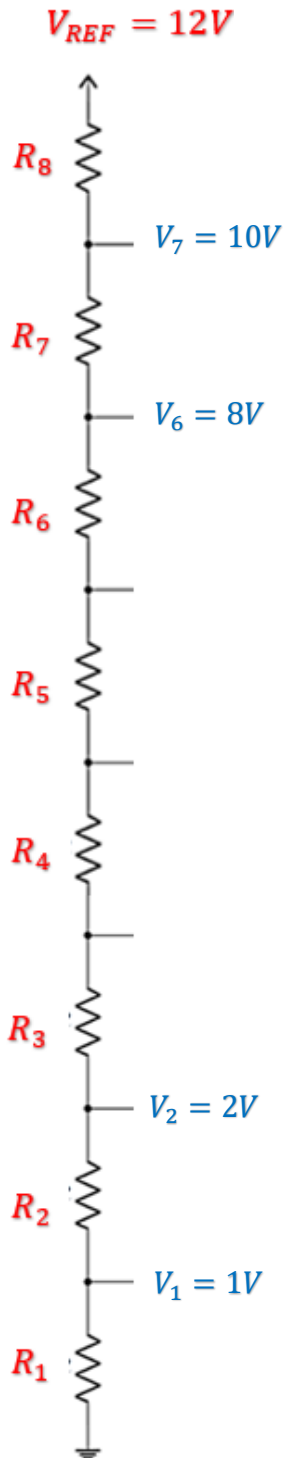- Since there are 8 levels: The ADC is a 3-bit ADC
- Therefore, we will need 8 resistors and  $(8-1) = 7$  op-amps
- Vref will have to be the highest shown voltage in the transfer curve
- We only show the resistor network below which is connected to the op-amps:



- In design problems, we have the freedom to choose some values. We first find the relations between the resistors:

$$V_1 = 1 = 12 \frac{R_1}{R_1 + R_2 + \dots + R_8} = 12 \frac{R_1}{\sum R} \text{ [Voltage division]}$$

$$\Rightarrow R_1 = \frac{1}{12} \sum R \text{ (here, } V_1 = 1 \text{ comes from the transfer curve)}$$

$$\text{Similarly, } V_2 = 2 = 12 \frac{R_1 + R_2}{\sum R} \Rightarrow R_1 + R_2 = \frac{1}{6} \sum R$$

$$\Rightarrow \left( \frac{1}{12} \sum R \right) + R_2 = \frac{1}{6} \sum R \Rightarrow R_2 = \frac{1}{12} \sum R$$

Same process for,  $V_3$ , then  $V_4 \dots \dots \dots$ , then  $V_7$ .

- In this way, we find all 8 resistor values in terms of  $\sum R$  = the total equivalent resistor. But,  $\sum R$  itself does not have a value yet. Here, we have a freedom of assuming any value we want.
- Assume,  $\sum R = 60k\Omega$  (any value you like). Then find the 8 resistor values. In this way, the resistors will maintain the transfer curve for the ADC.
- Finally, draw the entire flash ADC to complete the design.

Q3	<p>Draw the Digital Input vs <math>V_{in}</math> curve (Transfer curve) of a 3-bit Flash ADC which has the resistor network below.</p> <p><b>Hint:</b> find all of the node voltages (<math>V_1, V_2, \dots, V_7</math>) using any circuit theorems: KVL/ Nodal/Voltage division. [<i>Practice yourself</i>]</p>
----	--

Given,

$$R_1 = R_3 = R_5$$

$$R_2 = R_4 = R_6$$

$$R_7 = 2R_8$$

$$R_1 = 3R_2 = 2R_7 = 12k\Omega$$

