

$$V_3 = I(R_2 + R_3 + R_4) = \frac{V_{REF}}{4R} \times \frac{5R}{2} = 5 \times \frac{V_{REF}}{8} \quad (5)$$

Now, closely analyze the operation of all the op-amps. OA1 has input voltage V_A at its '+' input (non-inverting input) and V_1 at '-' input (inverting input). If $V_A > V_1$, OA1 will give a HIGH output. Similarly, OA2 will give HIGH output if $V_A > V_2$ and OA3 if $V_A > V_3$.

Next, we send the outputs of all the op-amps to a priority encoder. We will then get our desired 2-bit digital signal at the output of this encoder which corresponds to the original analog input signal.

For this flash ADC design, we will need $2^n - 1$ op-amps for implementing an n -bit ADC. This presents a huge disadvantage in terms of practical implementation in laboratory.

Procedure:

1. Construct the circuit as shown in figure 1. Consider, $R = 10 \text{ K}\Omega$.
2. We will not use any external LEDs. Connect the outputs of the encoder to the LEDs of the Trainer Board.
3. Vary the analog input voltage, V_{IN} or, V_A from 0V to 5V.
4. Observe when the two LEDs switches ON or OFF and measure the input voltage which causes the transitions. Fill up data table 1 using these data.

Note : The encoder is "Active LOW". This means that whenever the output (A_0, A_1) is supposed to be "Logical 1", they are at a LOW voltage. Hence, the corresponding LED will turn OFF!

Data Tables

Fill up the table for the Flash AD Converter.

Input Voltage $V_{IN} = V_A$	State of LED1	State of LED0	Digital Binary Output
0.74	ON	ON	00
1.14	ON	OFF	01
3.172	OFF	ON	10
5	OFF	OFF	11

Table 1: Data Table for Flash AD Converter

Signature

Report

Please answer the following questions briefly in the given space.

1. Use your "group number" as input voltage V_A and observe the output. If group number is greater than 5, divide by 2 and use the resultant value as input. Explain the reason for obtaining the output.

Ans. Group member = 4 Here, $V_0 = \square$ $A_0 = 0.02V$
 $A_1 = 0.025V$
 $\therefore V_A = 4$

Here,

$$I = \frac{5-0}{4R} = \frac{5}{4} R$$

$$V_1 = I \frac{R}{2} = 0.625$$

$$V_2 = I \frac{3R}{2} = 1.375$$

$$V_3 = I \frac{5R}{2} = 3.125$$

Now, $V_A > V_3$

\therefore All the comparators will be ON.

2. Adjust the input voltage such that we get Binary output 00 and 01. For each case, measure the output voltages of the encoder. Explain why the LEDs turn on or off. (Note: disconnect the LEDs when measuring the output voltages)

Ans. LED, at output 00, output voltage = 0.613V

LED, at output 01, output voltage = 0.847V

LED, turned ON and OFF depending on the binary output when both LED have the output 00, the LED is ON.

3. Write down an advantage and disadvantage of Flash AD converter.

Ans. Advantage: Flash ADC is the fastest analog to digital converter. It converts an analog signal to a digital signal within one clock cycle.

Disadvantage: It needs a lot of components to do its operations. So, it is quite costly. It also consumes substantial quantity of power.

4. Measure the voltages of points V_3 , V_2 and V_1 . Do the values match with the theory?

Ans. Here,

$$V_3 = 3.138 \text{ V}$$

$$V_2 = 1.885 \text{ V}$$


$$V_1 = 0.628 \text{ V}$$

The values does not match with the theory.

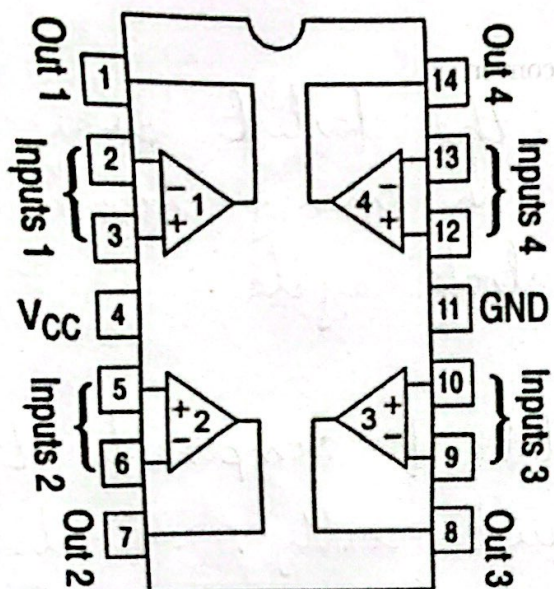
5. If we wanted to build a 3-bit Flash AD converter, how many resistors and comparators (op-amps) would we need?

Ans.

For a 3-bit flash AD converter, we would need $2^3 - 1 = 7$ resistors and $2^3 = 8$ comparators.



LM324 IC (Quad Op-Amp) pin diagram

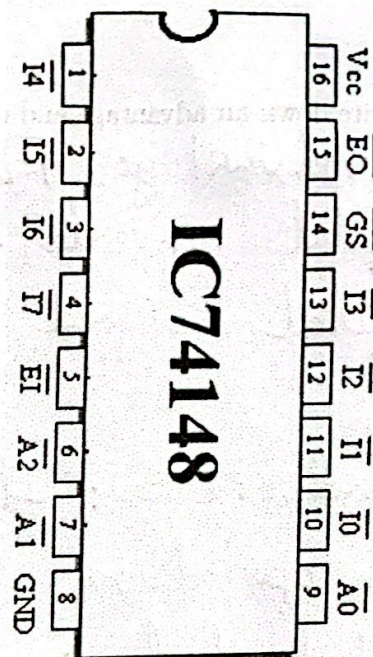

74148 IC (Encoder) pin diagram

	INPUTS								OUTPUTS		
EI	0	1	2	3	4	5	6	7	A2	A1	A0
H	X	X	X	X	X	X	X	X	H	H	H
L	H	H	H	H	H	H	H	H	H	H	H
L	X	X	X	X	X	X	X	L	L	L	L
L	X	X	X	X	X	X	L	H	L	L	H
L	X	X	X	X	X	L	H	H	L	H	L
L	X	X	X	X	L	H	H	H	L	H	H
L	X	X	X	L	H	H	H	H	H	L	L
L	X	X	L	H	H	H	H	H	H	L	H
L	X	L	H	H	H	H	H	H	H	H	L
L	L	H	H	H	H	H	H	H	H	H	H

74148 IC (Encoder) Truth Table